

# ESE 461: Design Automation for Integrated Circuit Systems

## Homework 1

**Due: Sep 5th, 5:00pm, homework bin labeled “ESE461” in Green Hall**

---


---

1. Write the Boolean expression in Product of Sum (POS) form for the truth table to the right.  
Complete the Karnaugh Map and simplify the Boolean expression.

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

		BC			
		00	01	11	10
A	0				
	1				

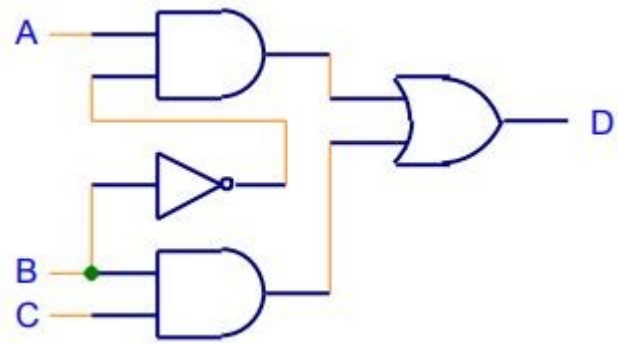
2. Given the following digital logic gates:



- Fill out the truth table for the circuit.
- What is the function of the circuit?

3. Design a combinational circuit that accept a 3-bit number and generates a 6-bit binary number output equal to the square of the input number. (Hint: first derive the truth table.)

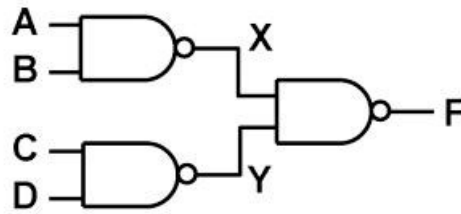4. Consider the following static CMOS logic design:



- c) Write down the Boolean expression for the logic function  $F$  using inputs  $A$ ,  $B$ ,  $C$ , and  $D$  implemented by the logic gates in the above figure.
- d) Give the circuit in above figure using static CMOS circuits for the individual logic gates (hint: each NAND gate can be composed of a two-input AND gate and a NOT gate). Be sure to label all inputs, outputs, and other circuit nodes.

5. Design a finite-state machine for a sequence detector that detects a sequence of 011 on a single input X. (Hint: first design the state representation, then derive the state transition diagram, and finally use the truth table to map out the combinational logic.)

***Required Reading Assignments:***

Textbook –

*Microelectronic Circuits (7th Edition), by Sedra & Smith*

Appendix 1

Chapter 5.1, 5.2, 15.1

*Digital Integrated Circuits (2<sup>nd</sup> Edition), by Jan M. Rabaey, Anantha Chandrakasan, Borivoje Nikolic.*

Chapter 2 (2.5 optional),

Chapter 3.3, 3.4 (optional)

***Required Video about integrated circuit (IC) fabrication and how transistor works:***

1. IC fabrication  
<https://www.youtube.com/watch?v=35jWSQXku74>  
<https://www.youtube.com/watch?v=AOaJFKWXY0>
2. How transistor works  
<https://www.youtube.com/watch?v=IcrBqCFLHIY>  
<https://www.youtube.com/watch?v=7ukDKVHnac4>

***Recommended optional video for in-depth understanding of transistor operation:***

Razavi Electronics Lecture 1, 2, 3

[https://www.youtube.com/watch?v=yQDfVJzEymI&list=PL7qUW0KPfsIIOPOKL84wK\\_Qj9N7gvJX6v&index=1](https://www.youtube.com/watch?v=yQDfVJzEymI&list=PL7qUW0KPfsIIOPOKL84wK_Qj9N7gvJX6v&index=1)

[https://www.youtube.com/watch?v=NWolpDgi6\\_Y&list=PL7qUW0KPfsIIOPOKL84wK\\_Qj9N7gvJX6v&index=2](https://www.youtube.com/watch?v=NWolpDgi6_Y&list=PL7qUW0KPfsIIOPOKL84wK_Qj9N7gvJX6v&index=2)

[https://www.youtube.com/watch?v=mhtYm-USVD8&index=3&list=PL7qUW0KPfsIIOPOKL84wK\\_Qj9N7gvJX6v](https://www.youtube.com/watch?v=mhtYm-USVD8&index=3&list=PL7qUW0KPfsIIOPOKL84wK_Qj9N7gvJX6v)